

1.) Reduce the state table to the minimum number of states by using the Implication table.

Current State	Next State		Outputs
	X=0	X=1	
A	D A	C	0
B	F	H	0
C	E C	D A	1
D	A	E	0
E	C	A	1
F	F	B	1
G	B	H	0
H	C	G	1

B	D-F E-H						
C	X	X					
D	<u>D-A</u> <u>C-E</u>	E-A H-E	X				
E	X	X	<u>E-C</u> <u>D-A</u>	X			
F	X	X	E-F D-B	X	C-F A-B		
G	D-B E-H	F-B H-G	X	A-B E-H	X	X	
H	X	X	E-C D-G	X	C-G A-G	F-G B-G	X
	A	B	C	D	E	F	G


Duplicate
D-A
C-E

Duplicates

D-A

C-E

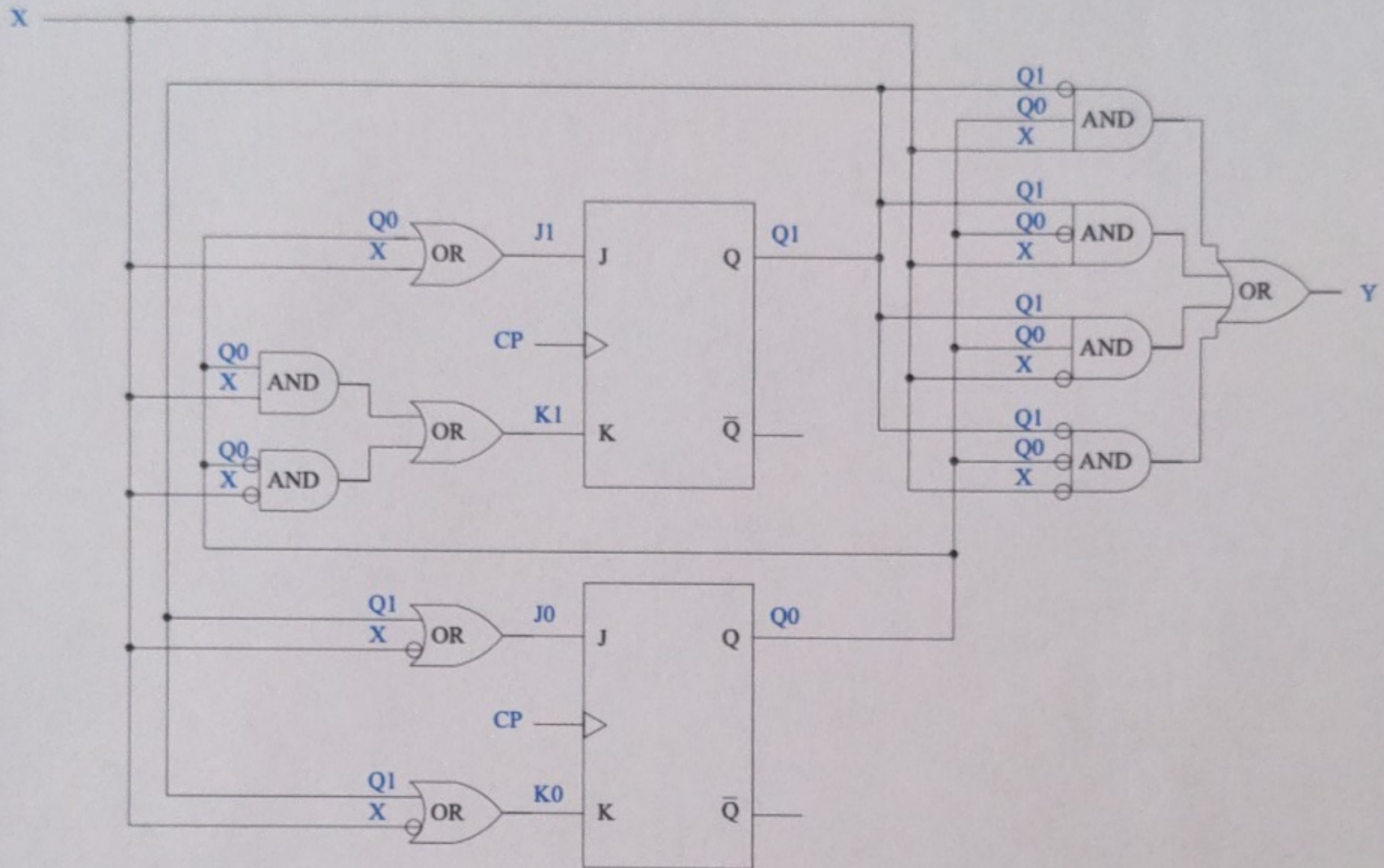2.) Deriving the state transition diagram from the schematic below.



a.) What type of state machine is this?

This is a Mealy Machine

b.) Write the Boolean equations for the output and the input to the flip-flops

$$Y = \bar{Q}_1 \cdot Q_0 \cdot X + Q_1 \cdot \bar{Q}_0 \cdot X + Q_1 \cdot Q_0 \cdot \bar{X} + \bar{Q}_1 \cdot \bar{Q}_0 \cdot \bar{X}$$

$$J_1 = Q_0 + X \quad K_1 = Q_0 \cdot X + \bar{Q}_0 \cdot \bar{X}$$

$$J_0 = Q_1 + \bar{X} \quad K_0 = Q_1 + \bar{X}$$

c.) Create next state and output tables.

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Current State			Input	Next State			Outputs	Flip Flop Inputs			
State Name	Q1	Q0	X	State Name	Q1(t+1)	Q0(t+1)	Y	J1	K1	J0	K0
A	0	0	0	C	1	0	1	1	X	0	X
A	0	0	1	C	1	0	0	1	X	0	X
B	0	1	0	A	0	0	0	0	X	X	0
B	0	1	1	C	1	0	1	1	X	X	0
C	1	0	0	B	0	1	0	X	1	1	X
C	1	0	1	B	0	1	1	X	1	1	X
D	1	1	0	C	1	0	1	X	0	X	0
D	1	1	1	A	0	0	0	X	1	X	0

d.) Draw the state transition diagram.

